CHANDERNAGORE COLLEGE

SEMESTER – I (NEP) B.Sc. HONOURS PRACTICAL EXAMINATION 2023

SUBJECT: COMPUTER SCIENCE COURSE CODE: COMP 1011

FULL MARKS: 20 COURSE NAME: COMPUTER FUNDAMENTALS AND DIGITAL LOGIC TIME: 1 HOURS

Q1 : Answer any 1 of the questions (10)

a) Prove NAND/NOR is Universal gate.

b) Implement X'OR and X'NOR Gate using Basic Gates.

c) Implement Full Adder.

D) Implement Full Subtractor.

Q2 : Viva (5)

Q3 : Lab Notebook (5)